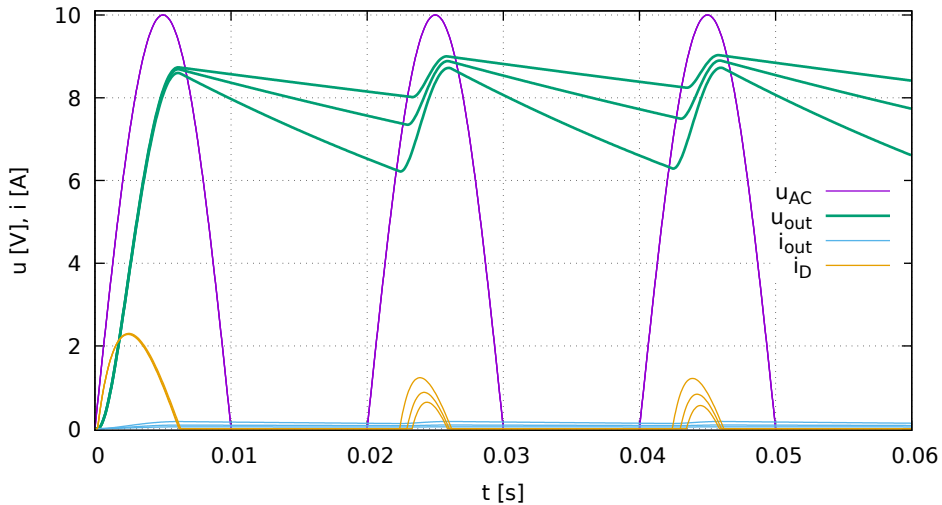


Rectifier ($U_{AC}=10V/50Hz$, $R_{AC}=1\Omega$, $C=1000\mu F$, $R_z = 50, 100, 200 \Omega$)



Rectifier ($U_{AC}=10V/50Hz$, $R_{AC}=1\Omega$, $C=1000\mu F$, $R_z = 50, 100, 200 \Omega$)

